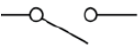
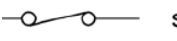
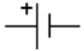
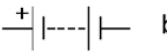

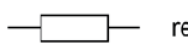
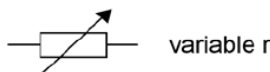
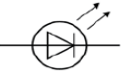

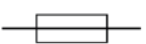
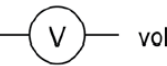

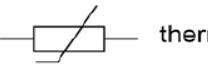
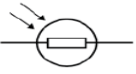


AQA P2a Electrical circuits
Triple - Physics

RP in this topic: ① resistance of wire ② resistors in series and parallel ③ I-V characteristics




 switch (open)	Breaks circuit; stopping the current
 switch (closed)	Completes circuit; allows current to flow
 cell	Store of chemical energy
 battery	Two or more cells
 diode	Only allows current to flow one way
 resistor	Fixed resistance reduces current
 variable resistor	Changeable resistance reduces current
 LED	Emits light
 lamp	Emits light
 fuse	Breaks circuit when current too high
 voltmeter	Measures potential difference
 ammeter	Measures current
 thermistor	Resistance decreases as temperature increases
 LDR	Resistance decreases as light intensity increases

Key word	Definition
Charge	The number of electrons. Measured in coulombs (C)
current	Flow of charge (the speed of electrons). Measured in amps (A)
Potential difference	(often abbreviated to p.d.) Energy per electron. Measured in volts (V)
resistance	The amount an object reduces the current. Measured in ohms (Ω)

Symbol equation	Word equation
$Q = I t$	Charge flow = current x time
$V = I R$	Potential = current x resistance difference

Series circuit	A single closed loop. Electrons pass through every component in turn.
Parallel circuit	Two or more closed loops.

	Series circuit rules	Parallel circuit rules
current	Same current through each component in the circuit	Add current in each loop and it will EQUAL the total current going into or out of the battery
Potential difference	P.d. of the power supply is shared by all the components	P.d. along EACH loop is EQUAL to the p.d. of the battery.
resistance	Add the resistance of each component and it will EQUAL the resistance of the whole circuit. So, $R_{total} = R_1 + R_2$	Each extra loop with resistance will reduce the overall resistance of the entire circuit.

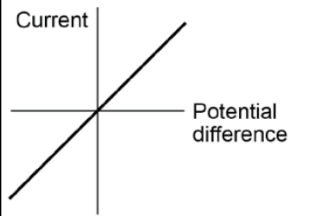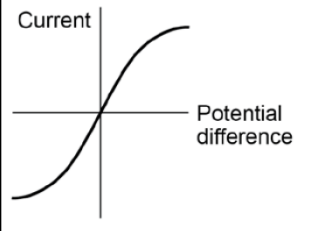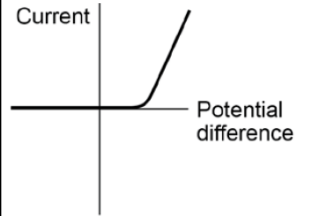	Fixed resistor I-V graph Called 'ohmic' because the resistance does not change. Current is directly proportional to p.d.
	Filament lamp I-V graph Resistance increases as temperature increases. Current increases as p.d. increases but the increases becomes less and less.
	Diode I-V graph In one direction as p.d. increases the current increases. But when the p.d. is reversed the current remains zero when the p.d. increases

Thermistor - Resistance decreases as temperature increases so current increases. Used to change the current in circuits e.g. thermostat automatically controls the temperature at home.

Light dependent resistor - Resistance decreases as light intensity increases so current increases. Used to change the current in circuits e.g. street lights automatically switch on when it gets dark.

AQA P2a Electric fields and static electricity
Triple - Physics

There are no RPs in this section

Static charge – charge can build up on an insulated object.

When 2 insulators are rubbed together, electrons move from one object to another.

Object loses electrons – becomes positively charged

Object gains electrons – becomes negatively charged

Electrostatic force – is a non contact force	Same charge	repel
	Opposite charge	attract

Potential difference and current









Potential difference causes a current to flow.
Power supplies provide a p.d. Current will always flow from a high p.d. to a low p.d.

Electric shocks

If you touch something with a high p.d., current will pass through you into the ground (0V p.d.)

Key word	Definition
charge	The number of electrons. Measured in coulombs (C)
current	Flow of charge (the speed of electrons). Measured in amps (A)
potential difference	(often abbreviated to p.d.) Energy per electron . Measured in volts (V)
resistance	The amount an object reduces the current. Measured in ohms (Ω)

Diagrams of charged spheres

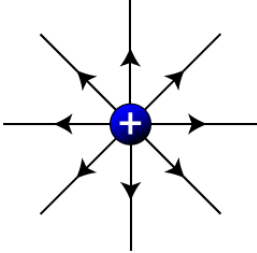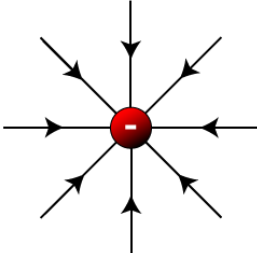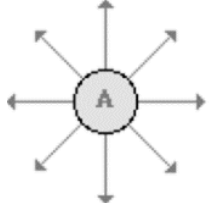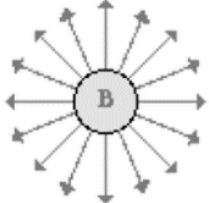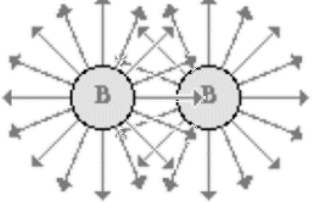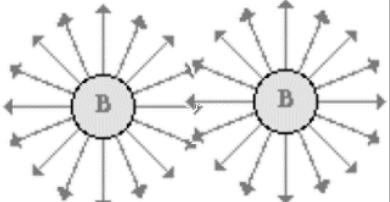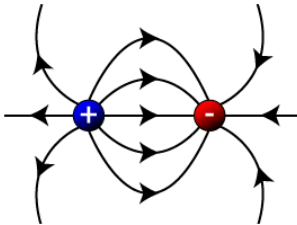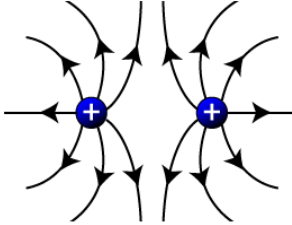positive charge	negative charge	Arrow direction
		Positively charged – arrows point away Negatively charged – arrows point towards
weak charge	strong charge	Density of field lines
		A - weaker charge so less field lines B - stronger charge so less field lines
closer together	further apart	Force is stronger when closer
		When 2 charged particles are closer the force is stronger because there are more field lines interacting.
attraction	repulsion	Pairs of charged particles
		Showing fields lines during attraction and repulsion